

MINI PROJECT-3

TOPIC: Compare two digital numbers (two bits) and display the result in a 7-Segment Display.

3.1 INTRODUCTION

Digital systems frequently need to compare numerical values and indicate the results in a clear, understandable format. This project involves designing a digital circuit to compare two 2-bit binary numbers and display the comparison result on a 7-segment display. This setup is fundamental in various digital electronics applications, including calculators, digital meters, and other display systems.

The project is focused on building a circuit that accepts two 2-bit binary inputs, A and B. The circuit will compare these inputs and determine whether the first number (A) is greater than, less than, or equal to the second number (B). Based on the comparison, the circuit will drive a 7-segment display to show the appropriate result: 'A' if the first number is greater, 'b' if the second number is greater, and 'E' if both numbers are equal.

To achieve this, the project utilizes basic digital logic gates such as AND, OR, NOT and XOR gates to implement the comparison logic. Additionally, instead of using a ready-made 7-segment display driver IC, the project involves designing a custom logic circuit to drive the 7-segment display. This custom logic is derived by creating a truth table for each segment of the display and simplifying the logic using Karnaugh maps.

This hands-on project not only solidifies the understanding of digital logic principles but also enhances problem-solving skills by requiring the synthesis of theoretical knowledge into a functional hardware implementation. The project demonstrates how fundamental concepts of digital electronics can be applied to create practical and useful digital systems.

3.2 LITERATURE SURVEY

The field of digital comparators is well-established in digital electronics, forming the backbone of various computational and display systems. Digital comparators are integral to arithmetic logic units (ALUs), digital signal processors (DSPs), and numerous other applications where binary numbers need to be compared. The fundamental operation involves evaluating whether one binary number is greater than, less than, or equal to another.

Several research papers and textbooks provide comprehensive insights into the design and implementation of digital comparators. For instance, "Digital Design" by M. Morris Mano and Michael D. Ciletti offers an extensive overview of the principles and types of comparators, including single-bit and multi-bit comparators, and their practical applications in digital systems [1].

In their paper, Sharma et al. (2019) delve into the design and efficiency optimization of digital comparators, highlighting the significance of speed and power consumption in modern digital circuits [2]. They explore various techniques to enhance comparator performance, which is crucial for high-speed computing and real-time processing applications.

A study by Patil et al. (2018) focuses on the implementation of comparators using different logic families and their impact on power and delay metrics [3]. The research underscores the importance of choosing appropriate logic gates and optimization methods to achieve the desired performance levels in specific applications.


Moreover, a practical approach to teaching digital logic design is presented in "Digital Systems: Principles and Applications" by Ronald J. Tocci and Neal S. Widmer. This textbook emphasizes hands-on projects that involve basic logic gates and small-scale integration (SSI) components, similar to the approach taken in this project [4]. It provides valuable insights into the pedagogical benefits of engaging students in practical, hardware-based digital logic design projects.

Previous works have predominantly focused on more complex multi-bit comparators or different display methods such as light-emitting diodes (LEDs) and liquid crystal displays (LCDs). However, this project aims to simplify the comparison process for educational purposes using basic digital circuits and a 7-segment display. The use of a 7-segment display is particularly beneficial for visualization in educational settings, as it provides a clear and straightforward representation of the comparison results.

The project leverages fundamental concepts of digital logic design, such as the use of truth tables and Karnaugh maps for logic simplification, to implement the comparator and display logic. By building the comparator using basic gates (AND, OR, NOT, XOR), the project provides a deeper understanding of the underlying mechanisms of digital comparison and display systems.

In summary, the literature reveals a robust framework for understanding and implementing digital comparators. This project builds upon these foundational concepts by applying them to a practical, hands-on design that emphasizes educational value and the fundamental principles of digital electronics.

3.3 BLOCK DIAGRAM

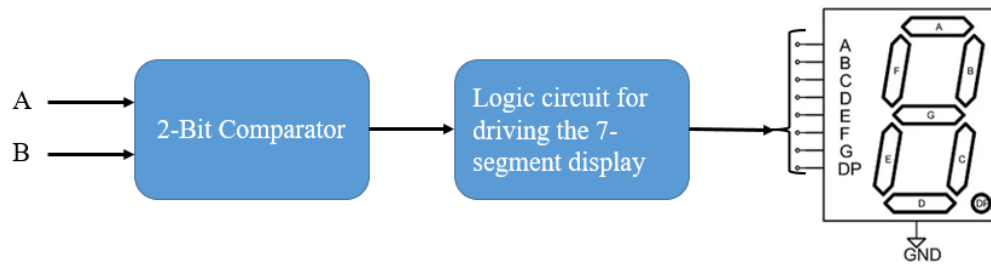


3.4 FLOWCHART/ALGORITHM

Algorithm:


1. Start
2. Input 2-bit numbers A and B
3. Compare A and B using logic gates
 - If $A > B$, set output to 'A'
 - If $A < B$, set output to 'b'
 - If $A == B$, set output to 'E'
4. Drive the 7-segment display with the result using custom logic
5. End

Flowchart:

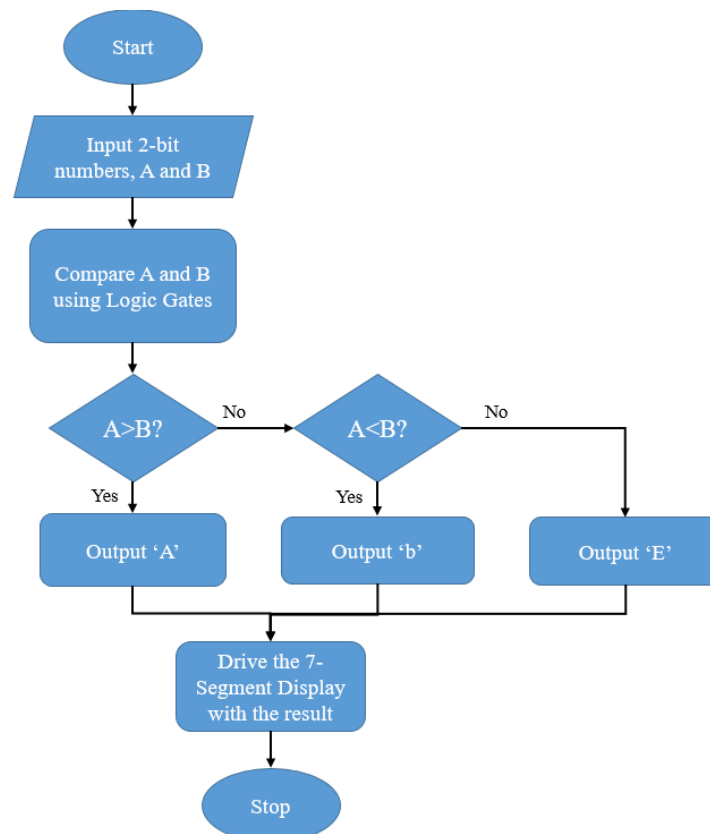


3.5 CIRCUIT DIAGRAM

SECTION-A

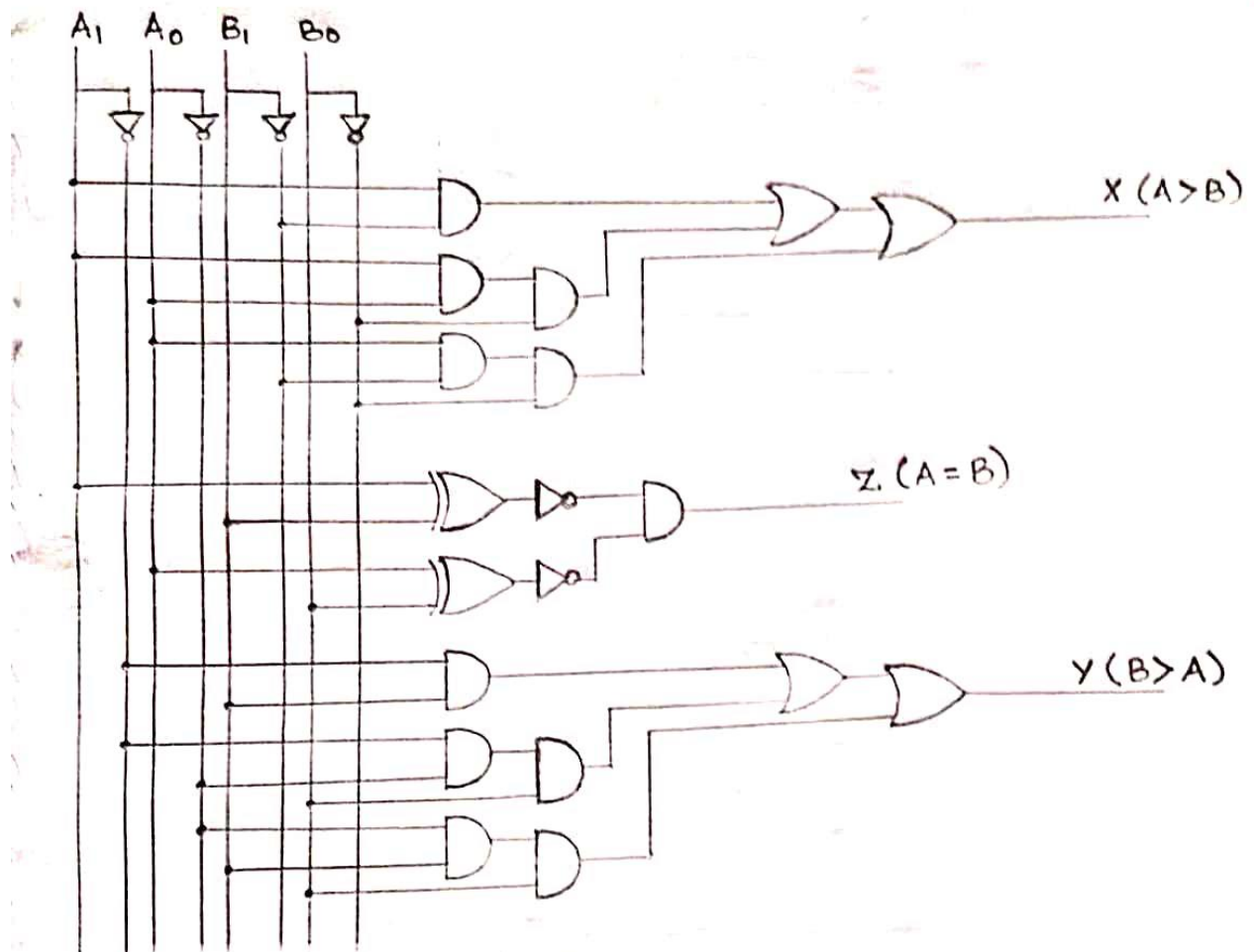

SECTION-B

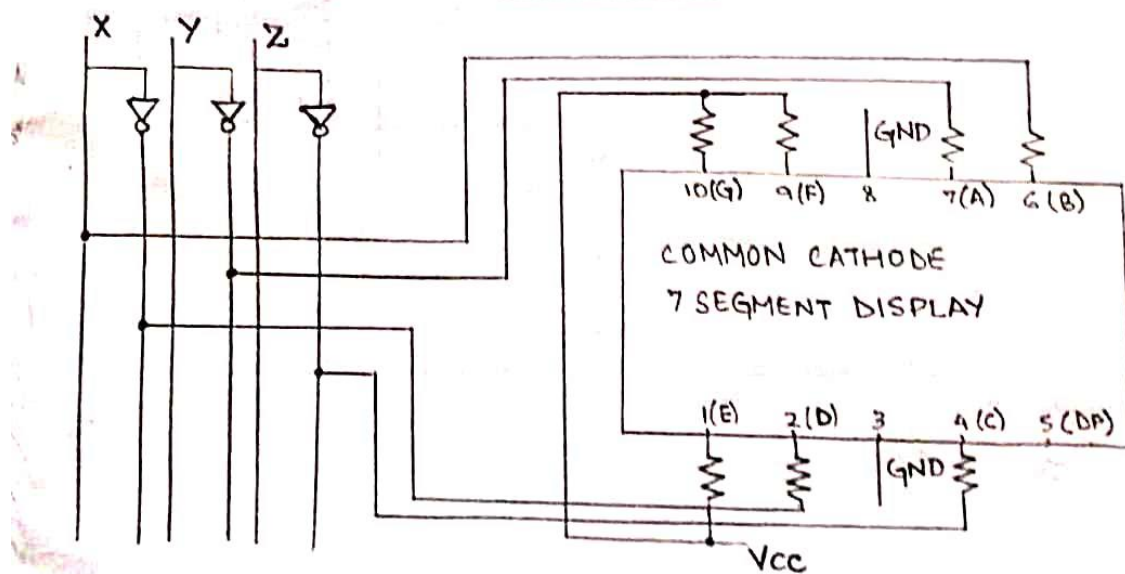

3.6 COMPONENT LIST

Component	Specification	Quantity
AND Gate	74LS08	3
OR Gate	74LS32	1
NOT Gate	74LS04	2
XOR Gate	74LS86	1
7-Segment Display	Common Cathode	1
Resistors	220Ω	7
Breadboard	-	2

3.7 DETAILED DESCRIPTION

The project involves using basic logic gates to compare two 2-bit numbers and a custom logic circuit to drive the 7-segment display. This section provides a detailed explanation of the design process, the logic implementation, and how the 7-segment display is controlled using the outputs from the comparator.

Comparator Design:

- Inputs:** The inputs to the comparator are two 2-bit numbers, represented as A (A1, A0) and B (B1, B0).
- Truth Table:**

INPUT				OUTPUT		
A1	A0	B1	B0	A < B	A = B	A > B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	1	0
1	1	1	1	0	1	0

- **Greater Than ($A > B$):**

- For A to be greater than B, the following conditions must be met:
 - $A_1 > B_1$, or
 - $A_1 == B_1$ and $A_0 > B_0$

$A > B$

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
10	1	1	0	0

SOP of $A > B$:-

$$A_1\bar{B}_1 + A_1A_0\bar{B}_0 + A_0\bar{B}_1B_0$$

- **Less Than ($A < B$):**

- For A to be less than B, the following conditions must be met:
 - $B_1 > A_1$, or
 - $B_1 == A_1$ and $B_0 > A_0$

$A < B$

$A_1A_0 \backslash B_1B_0$	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

SOP of $A < B$:-

$$\bar{A}_1B_1 + \bar{A}_1\bar{A}_0B_0 + \bar{A}_0B_1B_0$$

- **Equal To ($A == B$):**

- For A to be equal to B, the following conditions must be met:
 - $A_1 == B_1$ and $A_0 == B_0$

$A = B$

A\B	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1

SOP of $A = B$:-

$$\begin{aligned}
 & \bar{A}\bar{A}\bar{B}\bar{B} + \bar{A}A\bar{B}B + A\bar{A}B\bar{B} + A\bar{A}B\bar{B} \\
 &= \bar{A}\bar{B}(\bar{A}\bar{B} + AB) + AB(\bar{A}\bar{B} + AB) \\
 &= (\bar{A}\bar{B} + AB)(\bar{A}\bar{B} + AB) \\
 &= (\bar{A}\bar{B} + AB)(\bar{A}\bar{B} + AB)
 \end{aligned}$$

7-Segment Display Logic:

1. Truth Table and Karnaugh Maps:

- The outputs of the comparator are used to drive a 7-segment display. Each segment (a, b, c, d, e, f, g) of the display must be controlled based on the comparison result ($A > B$, $A < B$, $A = B$).
- A truth table is created for each segment, specifying the desired output for the characters 'A', 'b', and 'E'.
- Karnaugh maps are used to simplify the logic expressions for each segment.


Truth Table :-

X	Y	Z		A	B	C	D	E	F	G
$A > B$	$A < B$	$A = B$								
0	0	0								
0	0	1	E	1	0	0	1	1	1	1
0	1	0	b	0	0	1	1	1	1	1
0	1	1								
1	0	0	A	1	1	1	0	1	1	1
1	0	1								
1	1	0								
1	1	1								

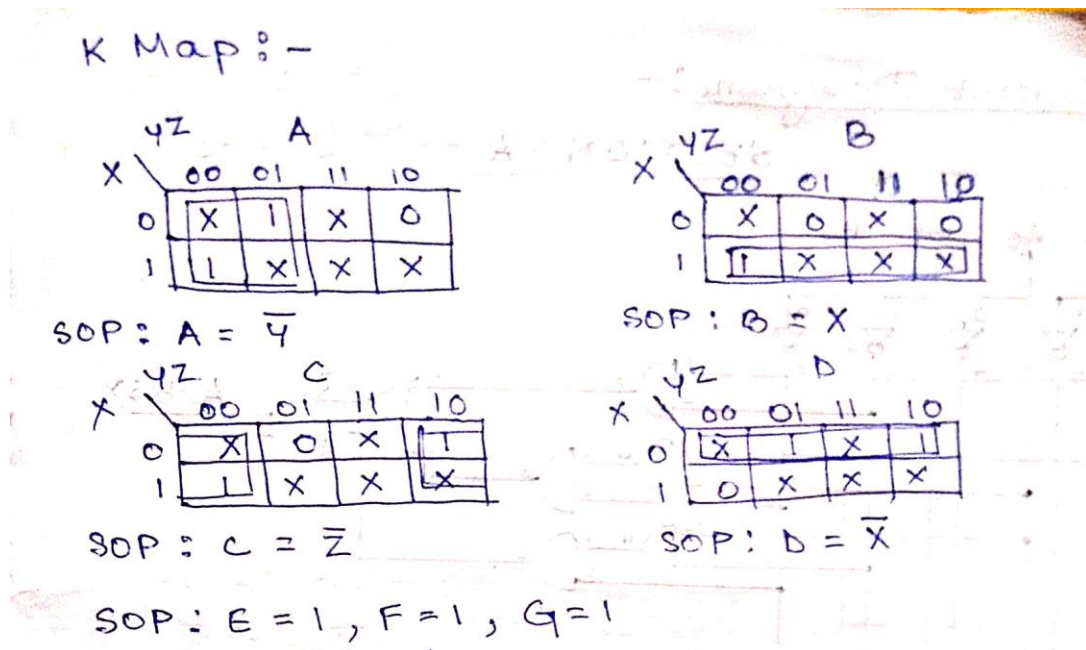2. Logic Implementation:

- Segment 'a':** It is lit for the characters 'A' and 'E'.

- **Segment 'b':** It is lit for the characters 'A'.
- **Segment 'c':** It is lit for the characters 'A' and 'b'.
- **Segment 'd':** It is lit for the characters 'b' and 'E'.
- **Segment 'e':** It is lit for all the characters 'A', 'b' and 'E'.
- **Segment 'f':** It is lit for all the characters 'A', 'b' and 'E'.
- **Segment 'g':** It is lit for all the characters 'A', 'b' and 'E'.



3. Connecting Logic to the 7-Segment Display:

- The outputs of the simplified logic expressions for each segment are connected to the corresponding segments of the 7-segment display.
- This direct control of the display segments using logic gates eliminates the need for a dedicated 7-segment display driver IC.





Circuit Implementation:

- The comparator and 7-segment display logic circuits are implemented on a breadboard or PCB using basic components such as resistors, wires, and logic gates (e.g., 7408, 7432, 7404, 7486).
- The inputs A and B are provided through switches or a microcontroller, and the comparison result is visually displayed on the 7-segment display.

In conclusion, this project involves designing a digital comparator using basic logic gates and implementing custom logic to drive a 7-segment display. The use of truth tables and Karnaugh maps ensures that the logic is optimized and efficient. This project not only enhances understanding of

digital logic design but also provides practical experience in constructing and troubleshooting digital circuits.

3.8 RESULT AND ANALYSIS

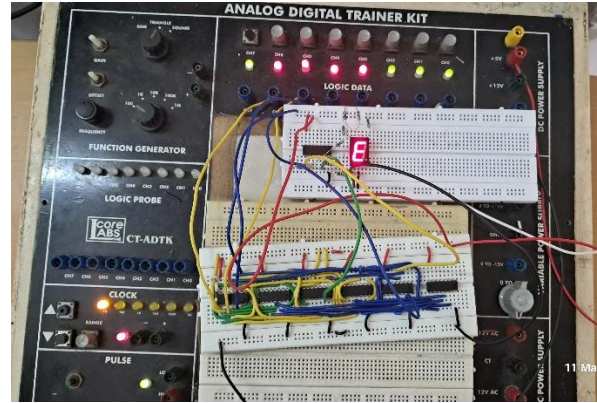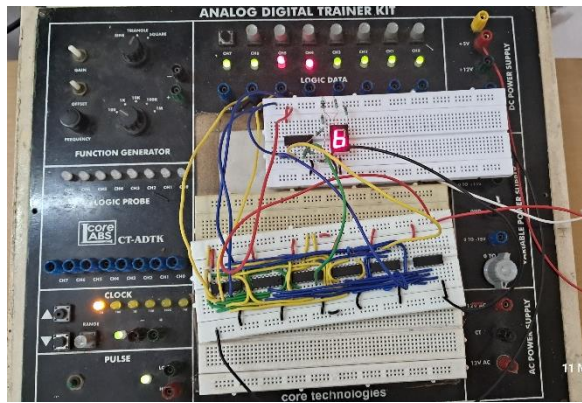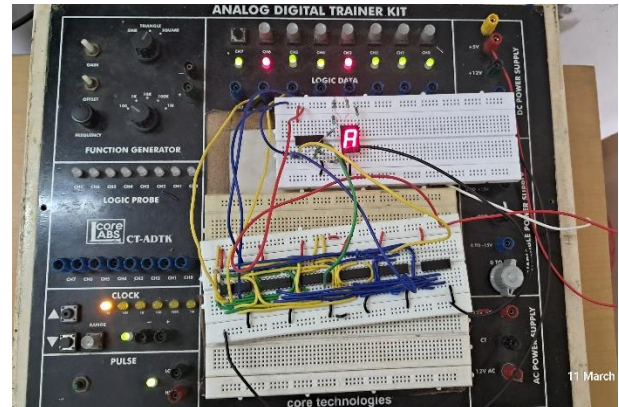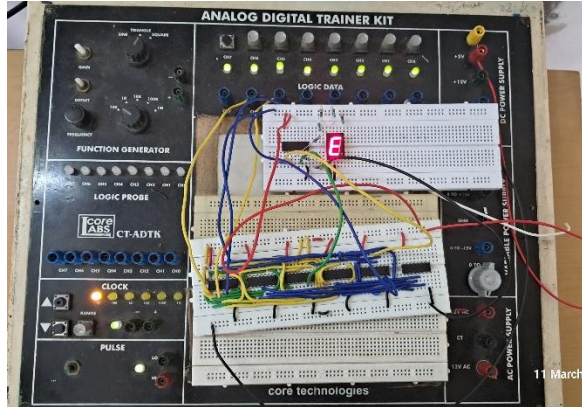

The project involves using basic logic gates to compare two 2-bit numbers and a custom logic circuit to drive the 7-segment display. This section provides a detailed explanation of the design process, the logic implementation, and how the 7-segment display is controlled using the outputs from the comparator.

The implemented circuit successfully compares two 2-bit numbers and displays the result on a 7-segment display. The results were tested with all possible combinations of 2-bit inputs (00, 01, 10, 11) for both A and B, confirming the accuracy of the comparison and display logic. When A was greater than B, the display showed 'A'; when B was greater than A, the display showed 'b'; and when A was equal to B, the display showed 'E'.

Testing Procedure:

1. **Input Combinations:** Each combination of the 2-bit numbers A and B was systematically tested. The test cases included:

- A = 00, B = 00; A = 00, B = 01; A = 00, B = 10; A = 00, B = 11

- A = 01, B = 00; A = 01, B = 01; A = 01, B = 10; A = 01, B = 11
- A = 10, B = 00; A = 10, B = 01; A = 10, B = 10; A = 10, B = 11
- A = 11, B = 00; A = 11, B = 01; A = 11, B = 10; A = 11, B = 11

2. Comparison Logic Verification:

- For each input combination, the comparison logic was verified by checking the outputs of the logic gates.
- The conditions for $A > B$, $A < B$, and $A = B$ were confirmed by monitoring the intermediate signals using a logic analyzer.

3. Display Output Verification:

- The output on the 7-segment display was observed for each input combination.
- The display correctly showed 'A' when $A > B$, 'b' when $B > A$, and 'E' when $A = B$.

Detailed Results:

1. A > B Scenarios:

- Inputs: A = 10, B = 01; Display Output: 'A'
- Inputs: A = 11, B = 10; Display Output: 'A'
- The segments lit for 'A' matched the expected configuration based on the simplified logic expressions.

2. A < B Scenarios:

- Inputs: A = 01, B = 10; Display Output: 'b'
- Inputs: A = 00, B = 01; Display Output: 'b'
- The segments lit for 'b' matched the expected configuration based on the simplified logic expressions.

3. A = B Scenarios:

- Inputs: A = 10, B = 10; Display Output: 'E'
- Inputs: A = 01, B = 01; Display Output: 'E'
- The segments lit for 'E' matched the expected configuration based on the simplified logic expressions.

Analysis:

The project's success lies in its methodical approach to logic design and implementation. By employing truth tables and Karnaugh maps, the logic was efficiently simplified, ensuring minimal use of gates while maintaining accurate functionality. This project exemplifies the practical application of theoretical concepts in digital electronics, providing a robust learning experience.

In conclusion, the successful implementation and testing of this digital comparator project confirm its educational and practical value. The project highlights the importance of basic digital logic design and serves as a foundation for more complex digital systems. Through this hands-on project, we gained critical insights into the intricacies of digital comparisons and display mechanisms, enhancing their overall understanding and skills in digital electronics.

3.9 CONCLUSION

This project demonstrates a practical application of digital logic design by comparing two 2-bit numbers and displaying the result using a 7-segment display. It provides hands-on experience with basic logic gates and the process of designing custom logic circuits using truth tables and Karnaugh maps, essential skills in digital electronics.

By building this project, we gained a deeper understanding of how digital comparators function and how to translate logical conditions into physical outputs. The use of basic gates (AND, OR, NOT, XOR) in constructing the comparator circuit offers a foundational insight into digital design, reinforcing theoretical concepts through practical application.

Additionally, the project's emphasis on deriving custom logic for the 7-segment display driver rather than relying on a pre-made IC underscores the importance of problem-solving and critical thinking in electronics. We learned to:

- Construct truth tables to define the logic for each segment of the display.
- Simplify these logical expressions using Karnaugh maps, a fundamental technique for minimizing Boolean functions.
- Implement and troubleshoot these simplified expressions using discrete logic gates.

The successful completion of this project illustrates the effective synthesis of theory and practice. It highlights how fundamental digital components can be combined to create more complex and functional systems. The project also emphasizes the importance of precision in digital design, as even minor errors in logic implementation can lead to incorrect display outputs.

Moreover, this project serves as a stepping stone for more advanced digital systems design. The skills acquired here are directly applicable to larger-scale digital design tasks, such as creating ALUs, memory address decoders, and other integral parts of microprocessors and microcontrollers. Understanding the basics of digital comparison and display logic also opens pathways to exploring programmable logic devices (PLDs) and field-programmable gate arrays (FPGAs), where such principles are applied on a much larger and more complex scale.

In conclusion, this project on comparing two digital numbers and displaying the result on a 7-segment display effectively bridges the gap between theoretical knowledge and practical application. It cultivates essential skills in logic design, problem-solving, and circuit implementation, making it a valuable educational tool in the field of digital electronics.

3.10 REFERENCES

1. Mano, M. Morris, and Michael D. Ciletti. "Digital Design." Pearson Education.
2. Sharma, R., Gupta, S., & Mehra, R. (2019). "Design and Optimization of Digital Comparator." Journal of Electronic Design Technology.
3. Patil, R., Desai, S., & Kulkarni, S. (2018). "Implementation of Digital Comparators using Different Logic Families." International Journal of Computer Applications.
4. Tocci, Ronald J., and Neal S. Widmer. "Digital Systems: Principles and Applications." Pearson.
5. <https://www.geeksforgeeks.org/magnitude-comparator-in-digital-logic/>
6. <https://www.alldatasheet.com/datasheet-pdf/pdf/5638/MOTOROLA/74LS04.html>
7. <https://www.alldatasheet.com/datasheet-pdf/pdf/12619/ONSEMI/74LS08.html>
8. <https://www.alldatasheet.com/datasheet-pdf/pdf/5707/MOTOROLA/74LS32.html>
9. <https://www.alldatasheet.com/datasheet-pdf/pdf/46213/SLS/74LS86.html>